

# SLA Battery Monitor Formulae

## Arduino ADC Calculations

Basic formula to calculate the unknown voltage on an analogue input:

$$V_{ADC} = \frac{V_{REF}}{2^{10}} \times ADC$$

$V_{ADC}$  = Unknown voltage on the analogue input.  
 $V_{REF}$  = Supply reference voltage ( $\approx 5v$ ).  
 $ADC$  = ADC reading on the analogue input.  
 $2^{10}$  = Number of ADC levels for a 10bit ADC.

Turning that around to have  $V_{REF}$  as the unknown:

$$V_{REF} = \frac{V_{ADC}}{ADC} \times 2^{10}$$

$V_{REF}$  = Unknown supply reference voltage.  
 $V_{ADC}$  = Voltage on the analogue input.  
 $ADC$  = ADC reading on the analogue input.

## Voltage Divider Calculations

$$I = \frac{V_I}{R_1 \times R_2}$$

$$V_O = \frac{I}{R_2}$$

$$V_O = V_I \times \frac{R_2}{R_1 \times R_2}$$

$I$  = Current through series resistors.  
 $V_I$  = Voltage In.  
 $V_O$  = Voltage Out.  
 $R_1$  = Top resistor.  
 $R_2$  = Bottom resistor.

